

Problem 2.6.1 - Part 1: Show that 1utmask 8000 implements a 4-input AND gate.

$$d = x_p$$

$$A = a \cdot b \cdot c \cdot d$$
$$A =$$

a	b	c	d	lut mark 0x8000
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
		0		0
		0		0
		0		0
1	1	1	1	1

Problem 2.6.1 - Part 2: Implement a 4-input XOR gate using LUT4.

a	b	c	d	F = a ¹ b ¹ c ¹ d ¹	
0	0	0	0	0	6 ← lutmask low bit
0	0	0	1	1	
0	0	1	0	1	
0	0	1	1	0	
0	1	0	0	1	9
0	1	0	1	0	
0	1	1	0	0	
0	1	1	1	1	
1	0	0	0	1	9
1	0	0	1	0	
1	0	1	0	0	
1	0	1	1	1	
1	1	0	0	0	6 ← lutmask high bits
1	1	0	1	1	
1	1	1	0	1	
1	1	1	1	0	

lutmask =
16'h 6996

= 0x6996

// Verilog:

```

module (F, a, b, c, d);
    input  a, b, c, d;
    output F;
    LUT4 #(16'h 6996) U(F, a, b, c, d);
endmodule
    
```


HW #2

Problem 2.6.1 - Part 3: Implement this function

using a LUT4:

$$f = a b c d + \bar{a} \bar{b} \bar{c} \bar{d} + a \bar{d} + \bar{a} b \bar{c} + \bar{b} d + \bar{a} b \bar{c} + a b \bar{c} d + b c d + \bar{a} c \bar{d}$$

- Each term tells which bits are set in the lutmask

a b c d	f	
0 0 0 0	1	$\bar{a} \bar{b} \bar{c} \bar{d}$
0 0 0 1	1	$\bar{b} d$
0 0 1 0	1	$\bar{a} c \bar{d}$
0 0 1 1	1	$\bar{b} d$
0 1 0 0	1	$\bar{a} b \bar{c}$
0 1 0 1	1	$\bar{a} b \bar{c}$
0 1 1 0	1	$\bar{a} c \bar{d}$
0 1 1 1	1	$b c d$
1 0 0 0	1	$a \bar{d}$
1 0 0 1	1	$\bar{b} d$
1 0 1 0	1	$a \bar{d}$
1 0 1 1	1	$\bar{b} d$
1 1 0 0	1	$a \bar{d}$
1 1 0 1	1	$a \bar{b} \bar{c} d$
1 1 1 0	1	$a \bar{d}$
1 1 1 1	1	$a b c d, b c d$

$$\text{lutmask} = 0 \times \text{FFFF}$$

$$= \boxed{16'h \text{ FFFF}}$$



// Verilog:

```
module (f, a, b, c, d);
    input a, b, c, d;
    output f;
```

```
    LUT4 #(16'h FFFF) u(f, a, b, c, d);
end module
```

// or: assign f = 1;

  Problem 2.6.2 - Part 1: Implement all possible 2-input functions using Actel Act1 block:





Function	a0	a1	s0	b0	b1	s1	s0	s1
1 xor(a,b)	0	1	b	1	0	b	a	0
2 and(a,b)	0	a	b	x	x	x	0	0
3 nand(a,b)	1	1	1	1	0	a	b	0
4 nor(a,b)	1	0	b	0	0	0	a	0
5 or(a,b)	0	0	0	1	1	1	a	b
6 xnor(a,b)	1	0	b	0	b	1	a	0
7 not(a)	1	0	a	x	x	x	0	0
8 not(b)	1	0	b	x	x	x	0	0
9 baf(a)	0	1	a	x	x	x	0	0
10 buf(b)	0	1	b	x	x	x	0	0
11 0 (contradiction)	0	0	0	0	0	0	0	0
12 a > b	a	0	b	x	x	x	0	0
13 a < b	b	0	a	x	x	x	0	0
14 a ≥ b	1	a	b	x	x	x	0	0
15 a ≤ b	1	b	a	x	x	x	0	0
16 1 (tautology)	1	1	1	1	1	1	1	1

Problem 2.6.2 - Part 2:
using an Act 1 block:

I implement this function

$$f = ab + \bar{b}c + d$$

  

```

// File: lutmask8000.v
// John Hubbard, 26 Jan 2015
// hw2 assignment for UCSC 30207: Digital Design with FPGA
//
// Part 1: show that lutmask 8000 implements a 4-input AND gate.

`timescale 1ns/1ns

module comparison(f, a, b, c, d);
    input a, b, c, d;
    output f;
    wire a, b, c, d, x, y, f;

    lutmask8000 U_lut(x, a, b, c, d);
    myAnd4      V_and(y, a, b, c, d);

    // This should have caused Vivado to remove the entire circuit, but it
    // did not. I don't understand why not. Both the elaborated design and the
    // schematic for the synthesized design showed that the AND4 and LUT4 were
    // still there.
    // --John Hubbard

    assign f = x ^ y;
endmodule

module lutmask8000(f, a, b, c, d);
    input a, b, c, d;
    output f;

    LUT4 #(16'h8000) U(f, a, b, c, d);
endmodule

module myAnd4(f, a, b, c, d);
    input a, b, c, d;
    output f;

    assign f = a & b & c & d;
endmodule

```

```

// File: lutmask8000_tb.v
// John Hubbard, 26 Jan 2015
// hw2 assignment for UCSC 30207: Digital Design with FPGA
//
// Part 1: show that lutmask 8000 implements a 4-input AND gate.

// Steps to run in ModelSim:
//
// cd D:/git_wa/classes/ucsc/fpga_30207/hw2/part1
// vlib work
// vlog *.v
// vsim work.lutmask_test
// add wave *
// run 100 ns
//

`timescale 1ns/1ns

module lutmask_test();
    reg a, b, c, d;
    reg [4:0] vec;
    wire lutmask_result, myAnd4_result, f_compare;

    lutmask8000 X(lutmask_result, a, b, c, d);
    myAnd4      Y(myAnd4_result,  a, b, c, d);
    comparison  Z(f_compare,      a, b, c, d);

    initial
    begin
        {a,b,c,d} = 4'b0;
        $display("abcd | lut4 | and4 | comparison");

        for (vec = 0; vec < 16; vec = vec + 1)
        begin
            #1 {a,b,c,d} = vec;

            #1 $display("%b%b%b%b | %b | %b | %b", a, b, c, d,
                lutmask_result, myAnd4_result, f_compare);

            if (f_compare)
                $display("Error: miscompare between lutmask8000 and myAnd4!");
        end
    end

endmodule


/* Sample run:

# run 1000ns
abcd | lut4 | and4 | comparison
0000 | 0    | 0    | 0
0001 | 0    | 0    | 0
0010 | 0    | 0    | 0
0011 | 0    | 0    | 0

```

0100		0			0			0
0101		0			0			0
0110		0			0			0
0111		0			0			0
1000		0			0			0
1001		0			0			0
1010		0			0			0
1011		0			0			0
1100		0			0			0
1101		0			0			0
1110		0			0			0
1111		1			1			0

* /

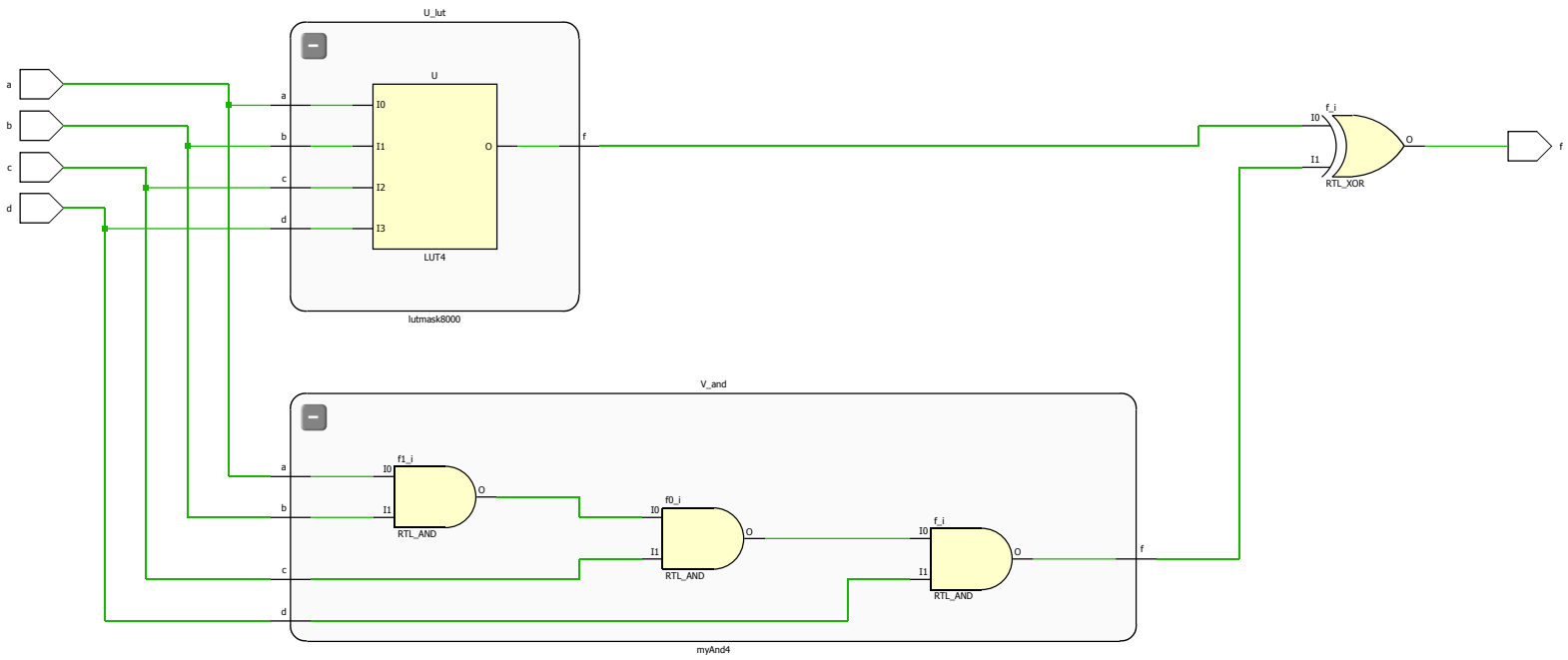

```

// File: various_lut4.v
// John Hubbard, 26 Jan 2015
// hw2 assignment for UCSC 30207: Digital Design with FPGA
//
// Problem 2.6.1, part 2: implement a 4-input XOR gate using a LUT4.
// Problem 2.6.1, part 3: Implement the function below using a LUT4:

`timescale 1ns/1ns

module comparison(f, a, b, c, d);
    input a, b, c, d;
    output f;
    wire a, b, c, d, x, y, f;

    xor_via_lut U_lut(x, a, b, c, d);
    myXor4      V_xor(y, a, b, c, d);

    assign f = x ^ y; // compare the results
endmodule

module xor_via_lut(f, a, b, c, d);
    input a, b, c, d;
    output f;

    // Problem 2.6.1, part 2: implement a 4-input XOR gate using a LUT4.
    //
    // Please see my paper notes for how the 0x6996 was derived:
    LUT4 #(16'h6996) U(f, a, b, c, d);
endmodule

module special_function_via_lut(f, a, b, c, d);
    input a, b, c, d;
    output f;

    // Problem 2.6.1, part 3: Implement the function below using a LUT4:
    //
    //  $f = a.b.c.d + a'.b'.c'.d' + a.d' + a'.b.c' +$ 
    //  $b'.d + a'.b.c' + a.b.c'.d + b.c.d + a'.c.d'$ 
    //
    // Please see my paper notes for how the 0xffff was derived:
    LUT4 #(16'hffff) U(f, a, b, c, d);
endmodule

module myXor4(f, a, b, c, d);
    input a, b, c, d;
    output f;

    assign f = a ^ b ^ c ^ d;
endmodule

```

```

// File: various_lut4_tb.v
// John Hubbard, 26 Jan 2015
// hw2 assignment for UCSC 30207: Digital Design with FPGA
//
// Problem 2.6.1, part 2: implement a 4-input XOR gate using a LUT4.
// Problem 2.6.1, part 3: Implement the function below using a LUT4:
//

`timescale 1ns/1ns

module various_luttests();
    reg a, b, c, d;
    reg [4:0] vec;
    wire xor_via_lut_result, myXor4_result, f_compare, special_result;

    xor_via_lut X(xor_via_lut_result, a, b, c, d);
    myXor4 Y(myXor4_result, a, b, c, d);
    comparison Z(f_compare, a, b, c, d);
    special_function_via_lut AA(special_result, a, b, c, d);

    initial
    begin
        {a,b,c,d} = 4'b0;
        $display("abcd | lut4 | xor4 | comparison | special_result");

        for (vec = 0; vec < 16; vec = vec + 1)
        begin
            #1 {a,b,c,d} = vec;

            #1 $display("%b%b%b%b | %b | %b | %b | %b", a, b, c, d,
                xor_via_lut_result, myXor4_result, f_compare, special_result);

            if (f_compare)
                $display("Error: miscompare between xor_via_lut and myXor4!");
        end
    end

endmodule

/* Sample run in Vivado's simulator (ModelSim cannot support LUT4):

# run 1000ns
abcd | lut4 | xor4 | comparison | special_result
0000 | 0 | 0 | 0 | 1
0001 | 1 | 1 | 0 | 1
0010 | 1 | 1 | 0 | 1
0011 | 0 | 0 | 0 | 1
0100 | 1 | 1 | 0 | 1
0101 | 0 | 0 | 0 | 1
0110 | 0 | 0 | 0 | 1
0111 | 1 | 1 | 0 | 1
1000 | 1 | 1 | 0 | 1
1001 | 0 | 0 | 0 | 1
1010 | 0 | 0 | 0 | 1

```



```
1011 | 1      | 1      |      0 | 1
1100 | 0      | 0      |      0 | 1
1101 | 1      | 1      |      0 | 1
1110 | 1      | 1      |      0 | 1
1111 | 0      | 0      |      0 | 1
*/
```